

1.4.3

BOOLEAN ALGEBRA

TOPIC WISE EXAM QUESTIONS

ANSWERS

A-LEVEL

OCR

6	(a)	(i) <ul style="list-style-type: none"> $\neg (A \vee B)$ // NOT (A OR B) $\underline{\vee} C$ // XOR C 	2 First MP requires brackets, NOT A or B is incorrect. Can be written in different order (e.g. C XOR NOT (B OR A) as long as logically correct. Accept $(A + B) \oplus C$																																								
6	(a)	(ii) <ul style="list-style-type: none"> 1 mark for first two rows (1,0) 1 mark for next two rows (0,1) 1 mark for next four rows (0,1,0,1) <table border="1" data-bbox="316 663 847 1077"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>P</th> <th>Marking Guidance</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>1</td> <td rowspan="2">1 Mark</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td rowspan="2">1 Mark</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td rowspan="4">1 Mark</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	A	B	C	P	Marking Guidance	0	0	0	1	1 Mark	0	0	1	0	0	1	0	0	1 Mark	0	1	1	1	1	0	0	0	1 Mark	1	0	1	1	1	1	0	0	1	1	1	1	3
A	B	C	P	Marking Guidance																																							
0	0	0	1	1 Mark																																							
0	0	1	0																																								
0	1	0	0	1 Mark																																							
0	1	1	1																																								
1	0	0	0	1 Mark																																							
1	0	1	1																																								
1	1	0	0																																								
1	1	1	1																																								
6	(b)	<ul style="list-style-type: none"> Correct highlighting on K map as shown $\neg A \wedge \neg C$ // $\bar{A} \bar{C}$ // NOT A AND NOT C... $A \wedge \neg D$ // $A \bar{D}$ // A AND NOT D... ...v // + // OR joining the 2 correct expressions together 	4 <table border="1" data-bbox="979 1211 1530 1720"> <thead> <tr> <th colspan="2" rowspan="2"></th> <th colspan="4">AB</th> </tr> <tr> <th>00</th> <th>01</th> <th>11</th> <th>10</th> </tr> </thead> <tbody> <tr> <th rowspan="4">CD</th> <th>00</th> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <th>01</th> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <th>11</th> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <th>10</th> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>Do not penalise candidates who attempt to simplify even further (e.g. NOT A AND NOT C = NOT (A OR C) using De Morgan's).</p> <p>MP1 - correct answer only</p> <p>MP4 is dependent on MP2 & 3</p>			AB				00	01	11	10	CD	00	1	1	1	1	01	1	1	0	0	11	0	0	0	0	10	0	0	1	1									
		AB																																									
		00	01	11	10																																						
CD	00	1	1	1	1																																						
	01	1	1	0	0																																						
	11	0	0	0	0																																						
	10	0	0	1	1																																						

5 (a)

Solution:

		AB			
		00	01	11	10
CD	00	0	0	1	1
	01	0	0	1	1
	11	1	1	1	1
	10	0	0	1	1


1 mark per bullet up to a maximum of 4 marks:

- 1 mark for filling in the table correctly
- 1 mark for the group shown in red
- 1 mark for the group shown in green
- 1 mark for the simplified expression $A \vee (C \wedge D)$

4
AO2.1
(2)
AO2.2
(2)

Brackets are not required for the simplified expression

5 (b)

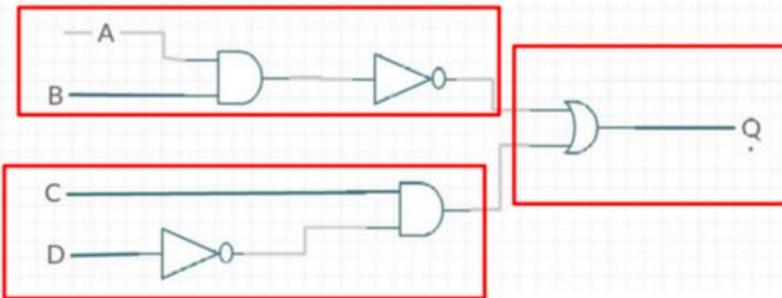

1 mark per bullet up to a maximum of 3 marks:

- An AND gate taking A and B as inputs with the output connecting to a NOT gate
- An AND gate taking C and the NOT of D as the inputs
- An OR gate taking the outputs of the NOT and AND gates

3
AO3.1
(3)

Allow NAND gate as alternative for BP1

5	(a)		$Q \equiv A \wedge B$ \wedge $(C \vee D)$	3	$Q \equiv A \wedge B \wedge (C \vee D)$ AO1.2 Accept alternative symbols for AND / OR e.g. $Q = A \text{ AND } B \text{ AND } (C \text{ OR } D)$ Brackets must be included for 3 rd point Allow XOR for bullet point 3 Any additional symbols max 2 marks																				
	(b)	i	<ul style="list-style-type: none"> Identification of De Morgan's and/or double negation rule Correct final answer to give $A \vee B$ 	2	AO2.2																				
	(c)	i	$S = A \vee B$ $C = A \wedge B$	2	AO2.1 Accept alternative symbols for AND /XOR																				
		ii	<ul style="list-style-type: none"> 1 mark for S column 1 mark for C column 	2	AO2.1 <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>A</th> <th>B</th> <th>S</th> <th>C</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> </tr> </tbody> </table>	A	B	S	C	0	0	0	0	0	1	1	0	1	0	1	0	1	1	0	1
A	B	S	C																						
0	0	0	0																						
0	1	1	0																						
1	0	1	0																						
1	1	0	1																						
		iii	<ul style="list-style-type: none"> Logic circuit adds together 2 binary digits / half adder 	4																					
			<ul style="list-style-type: none"> S gives sum, C gives carry Two half adders can be joined together... ...with an OR gate to form full adder 4 full adders can be used to add two four bit numbers Carry out on one joined to carry in on next 		AO1.2																				

4	(a)	i	<ul style="list-style-type: none"> left column filled with 1s ($\neg A \wedge \neg B$) ... right column filled with 1s ($A \wedge \neg B$)... ...Middle 2 columns filled with zero or blank 	3 AO1.2 (1) AO2.2 (2)	<p>AB</p> <table border="1"> <tr> <td></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td>00</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>01</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>11</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>10</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> </table>		00	01	11	10	00	1	0	0	1	01	1	0	0	1	11	1	0	0	1	10	1	0	0	1
	00	01	11	10																										
00	1	0	0	1																										
01	1	0	0	1																										
11	1	0	0	1																										
10	1	0	0	1																										
4		ii	<ul style="list-style-type: none"> $\neg B$ / NOT B Karnaugh map used to show 1s highlighted with overlap 	2 AO2.2	<p>AB</p> <table border="1"> <tr> <td></td> <td>00</td> <td>01</td> <td>11</td> <td>10</td> </tr> <tr> <td>00</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>01</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>11</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>10</td> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> </table>		00	01	11	10	00	1	0	0	1	01	1	0	0	1	11	1	0	0	1	10	1	0	0	1
	00	01	11	10																										
00	1	0	0	1																										
01	1	0	0	1																										
11	1	0	0	1																										
10	1	0	0	1																										
4	(b)	i	<ul style="list-style-type: none"> Delay / store a value... ...of 1 bit When a signal is given 	2 AO1.1																										
4	(b)	ii	<ul style="list-style-type: none"> Data input Clock input Q output When clock input goes high... ...Q changes to D NOT Q is reverse of Q 	4 AO1.1 (2) AO1.2 (2)																										

AS - Level



7						
	A	B	C	D	X	Marking Guidance
	0	0	0	0	0	1 Mark
	0	0	1	0	1	
	0	1	0	0	0	1 Mark
	0	1	1	0	1	
	1	0	0	0	0	1 Mark
	1	0	1	0	1	
	1	1	0	1	1	1 Mark
	1	1	1	1	0	

4
AO2.2 (4)
Award 1 mark for each group of 4 1's / 0's.



c	i	<table border="1"> <thead> <tr> <th>P</th> <th>S</th> <th>L</th> </tr> </thead> <tbody> <tr> <td>False</td> <td>False</td> <td>False</td> </tr> <tr> <td>False</td> <td>True</td> <td>True</td> </tr> <tr> <td>True</td> <td>False</td> <td>False</td> </tr> <tr> <td>True</td> <td>True</td> <td>False</td> </tr> </tbody> </table> <p>1 Mark for first 2 rows, 1 Mark for second 2 rows.</p>	P	S	L	False	False	False	False	True	True	True	False	False	True	True	False	2 AO1.2	Accept any sensible representation of True or False
	P	S	L																
False	False	False																	
False	True	True																	
True	False	False																	
True	True	False																	
	ii	<p>-P going into not Gate -S going into AND gate... -...NOT P going into AND gate, L coming out of it and no additional gates or connections. (1 per -, max 3)</p>	3 AO3.1																


AS - Level

9		<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>Q</th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table> <p>First 4 rows correct 1 mark Last 4 rows correct 1 mark</p>	A	B	C	Q	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	0	1	1	1	1	2 (AO2.2)	
	A	B	C	Q																																				
0	0	0	1																																					
0	0	1	1																																					
0	1	0	1																																					
0	1	1	1																																					
1	0	0	1																																					
1	0	1	1																																					
1	1	0	0																																					
1	1	1	1																																					

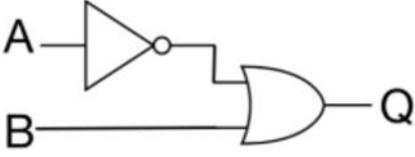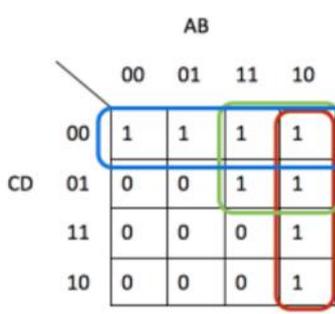10	a	 <p>- A going into NOT gate. - B and NOT A going into OR gate (and Q coming out of it) (1 Mark per -, Max 2)</p>	2 (AO1.2)	
	b	<p>- Groups correctly identified (with no further groups). - Answer includes $\neg C \wedge \neg D$ - Answer includes $A \wedge \neg B$ - Answer includes $A \wedge \neg C$ - All three sections joined with \vees in any order but with no further sections. E.g. $(A \wedge \neg B) \vee (A \wedge \neg C) \vee (\neg C \wedge \neg D)$ The brackets aren't necessary (1 Mark per -, Max 5)</p>	5 (AO1.2)	

AS - Level

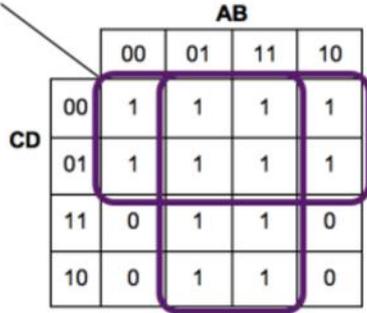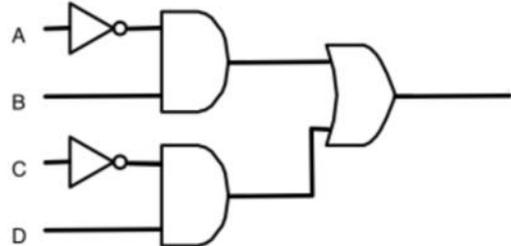6	a	 <p>Gives: $B \vee \neg C$</p> <p>- Correct two groups identified. - $B \vee$ - $\neg C$ (1 per -, max 3)</p>	3 AO2.1 (1, 1st Mark) AO2.2 (2, Last 2 Marks)	<p>Also accept: $\neg C \vee B$ Accept alternative symbols.</p>
	b	<p>- NOT gates after A and C - AND gates: one taking (NOT) A, B as inputs the other taking (NOT) C, D as inputs. - An OR gate taking in the outputs of both AND gates. - ...No further gates or connections (1 per -, max 4)</p>	4 AO2.2 (4)	

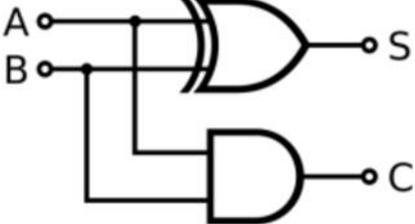4	a	<p>$Q \equiv (A \wedge B) \vee (C \wedge D)$</p> <p>1 mark for $(A \wedge B)$</p> <p>1 mark for $(C \wedge D)$</p> <p>1 mark for the \vee joining the two parts.</p>	3 (AO1.2)	<p>Accept $(C \wedge D) \vee (A \wedge B)$</p> <p>Accept $(B \wedge A)$ instead of $(A \wedge B)$</p> <p>Accept $(D \wedge C)$ instead of $(C \wedge D)$</p> <p>Accept alternative notations (e.g. +/. OR/AND)</p> <p>Accept AB as $(A.B)$ and CD as $(C.D)$</p> <p>Accept answers without brackets</p>																																																															
b	i	<table border="1" data-bbox="268 645 922 864"> <thead> <tr> <th>E</th> <th>F</th> <th>G</th> <th>$(E \wedge F)$</th> <th>$(E \wedge G)$</th> <th>$(E \wedge F) \vee (E \wedge G)$</th> <th>4</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>1</td> <td>(AO1.2)</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> <td>0</td> <td>1</td> <td>1</td> <td></td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>0</td> <td>1</td> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> <tr> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td>0</td> <td></td> </tr> </tbody> </table> <p>1 mark for each of the pairs of rows.</p>	E	F	G	$(E \wedge F)$	$(E \wedge G)$	$(E \wedge F) \vee (E \wedge G)$	4	1	1	1	1	1	1	(AO1.2)	1	1	0	1	0	1		1	0	1	0	1	1		1	0	0	0	0	0		0	1	1	0	0	0		0	1	0	0	0	0		0	0	1	0	0	0		0	0	0	0	0	0			
E	F	G	$(E \wedge F)$	$(E \wedge G)$	$(E \wedge F) \vee (E \wedge G)$	4																																																													
1	1	1	1	1	1	(AO1.2)																																																													
1	1	0	1	0	1																																																														
1	0	1	0	1	1																																																														
1	0	0	0	0	0																																																														
0	1	1	0	0	0																																																														
0	1	0	0	0	0																																																														
0	0	1	0	0	0																																																														
0	0	0	0	0	0																																																														
	ii	<p>$(F \vee G) \wedge E$</p> <p>One mark for the $(F \vee G)$</p> <p>One mark for the $\wedge E$</p>	2 (AO2.2)	<p>Accept:</p> <p>$(G \vee F) \wedge E$</p> <p>$E \wedge (F \vee G)$</p> <p>$E \wedge (G \vee F)$</p>																																																															
11	a	 <p>XOR Gate (1)</p> <p>AND Gate (1)</p> <p>Correct connections and no additional gates (1)</p>	3 (AO1,1)																																																																

11 b

- Correctly identified groups on Karnaugh map/Correct boolean statement.(1)
- NOT A AND NOT C Gates (1)
- A AND C gates (1)
- Both sets of gates joined by OR gate (with no other gates used). (1)


4

(AO2.2)

		AB			
		00	01	11	10
CD	00	1	1	0	0
	01	1	1	0	0
	11	0	0	1	1
	10	0	0	1	1

$$(\neg A \wedge \neg C) \vee (A \wedge C)$$

Or equivalent.

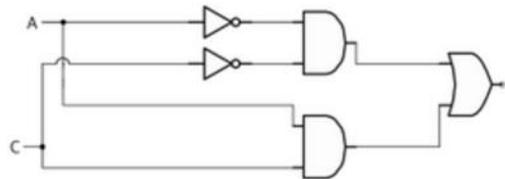



Or equivalent.

AS - Level

6	a		1 AO1.1	Accept diagram of gate only without input / output
	b	<p>OR gate outputs true if at least one of its inputs is true (1)</p> <p>XOR gate output true if and only if one of its inputs is true. (1)</p>	2 AO1.2	Accept appropriate, correctly labelled, truth tables. One mark for each truth table.

c	i	<table border="1"> <thead> <tr> <th>A</th> <th>B</th> <th>C</th> <th>D</th> <th>Output</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table>	A	B	C	D	Output	1	1	1	1	1	1	1	1	0	1	1	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	1	0	1	1	0	0	1	1	1	0	0	0	1	0	1	1	1	1	0	1	1	0	1	0	1	0	1	1	0	1	0	0	1	0	0	1	1	1	0	0	1	0	1	0	0	0	1	1	0	0	0	0	0	<p>4</p> <p>AO2.2</p> <p>1 Mark</p> <p>1 Mark</p> <p>1 Mark</p> <p>1 Mark</p>	
		A	B	C	D	Output																																																																																			
		1	1	1	1	1																																																																																			
		1	1	1	0	1																																																																																			
		1	1	0	1	1																																																																																			
		1	1	0	0	1																																																																																			
		1	0	1	1	1																																																																																			
		1	0	1	0	1																																																																																			
		1	0	0	1	1																																																																																			
		1	0	0	0	1																																																																																			
		0	1	1	1	1																																																																																			
		0	1	1	0	1																																																																																			
		0	1	0	1	1																																																																																			
		0	1	0	0	1																																																																																			
		0	0	1	1	1																																																																																			
		0	0	1	0	1																																																																																			
0	0	0	1	1																																																																																					
0	0	0	0	0																																																																																					

	ii	<p>$(A \vee B) \vee (C \vee D) \equiv \text{Output}$</p> <p>$A \vee B$ (1 Mark)</p> <p>$\vee (C \vee D)$ (1 Mark)</p>	<p>2</p> <p>AO2.2</p>	<p>Accept answer without brackets.</p> <p>Accept alternative notation i.e. OR , +</p>
--	----	--------------------------------------------------------------------------------------------------------------------------------------------------------	-----------------------	---------------------------------------------------------------------------------------

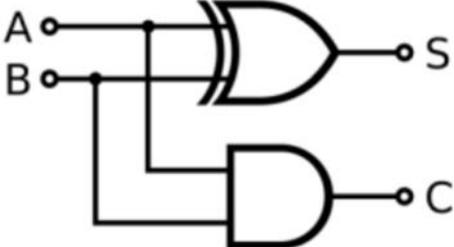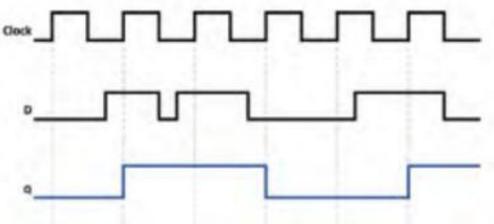1		 <p>XOR Gate (1)</p> <p>AND Gate (1)</p> <p>Correct connections and no additional gates (1)</p>	3 (AO1,1)	<p>Examiner's Comments Most candidates scored well on these questions demonstrating their understanding of logic gate circuits. Some candidates simplified the circuit in part b) which achieved full marks provided the resultant circuit gave the same output.</p>
5	i	A	1	
	ii	$\neg(A \vee B)$	1	
	iii	$A \vee B$	1	
4	a	To store the state of a bit	1	
	b	 <p>One mark for each two correct clock cycles.</p>	3	

6	a	i	<table border="1" data-bbox="373 237 699 533"> <thead> <tr> <th>A</th> <th>B</th> <th>C_{in}</th> <th>S</th> <th>C_{out}</th> </tr> </thead> <tbody> <tr><td>1</td><td>1</td><td>1</td><td>1</td><td>1</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>0</td><td>1</td></tr> <tr><td>0</td><td>1</td><td>0</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td></tr> <tr><td>0</td><td>0</td><td>0</td><td>0</td><td>0</td></tr> </tbody> </table> <p data-bbox="347 607 612 819"> 1 Mark for rows 1 and 2 1 Mark for rows 3 and 4 1 Mark for rows 5 and 6 1 Mark for rows 7 and 8 </p>	A	B	C _{in}	S	C _{out}	1	1	1	1	1	1	1	0	0	1	1	0	1	0	1	1	0	0	1	0	0	1	1	0	1	0	1	0	1	0	0	0	1	1	0	0	0	0	0	0	4	
A	B	C _{in}	S	C _{out}																																														
1	1	1	1	1																																														
1	1	0	0	1																																														
1	0	1	0	1																																														
1	0	0	1	0																																														
0	1	1	0	1																																														
0	1	0	1	0																																														
0	0	1	1	0																																														
0	0	0	0	0																																														
		ii	<ul style="list-style-type: none"> - Circuit adds two bits (and a carry bit) together / is an adder. - A B and C_{in} are added together - The result is given in S - And a carry bit in C_{out} (1 per -)	4																																														
	b	i	$S \equiv A \vee B \vee C_{in}$	1	Accept XOR instead of \vee Accept \oplus instead of \vee																																													
		ii	$C_{out} \equiv ((A \vee B) \wedge C_{in}) \vee (A \wedge B)$ <p data-bbox="347 1283 639 1375"> One mark for $((A \vee B) \wedge C_{in})$ One mark for $\vee (A \wedge B)$ </p>	2	Accept XOR instead of \vee Accept \oplus instead of \vee Accept AND instead of \wedge Accept OR instead of \vee Accept + instead of \vee																																													

**If you found this
useful, drop a follow
to help me out!**

THANK YOU!

GCST